# **ECE 385**

Spring 2019 Final Project Report

Game: Dr. Boom

A Game of Bomberman

Tingfeng Yan; Zerui An Section ABC / Tuesday 11:30 AM TAs: Zhenhong Liu, Gene Shiue

#### Introduction

This is our final project for this course, so we decide not to make something easy like a digital filter to just pass the final. We put our eyes on games because a game is one of the best forms to present. Considering what we've learnt so far, there are not many game forms to select from. Our final decision is to create a game like bomberman, and we call it Dr. Boom.


## **Description of Circuit**

The software part of our project is written in C code and runs on the NIOS II processor. It's only purpose is to collect key press information and pass it to the hardware.

The hardware part has several functions:

Keycode processor: interact with the software, decode the "purpose" of each key press. Game control: modify the characters and the map based on key press and other internal logic. Display: display the game board as well as scores and other parameters using VGA.

## **Block Diagram**

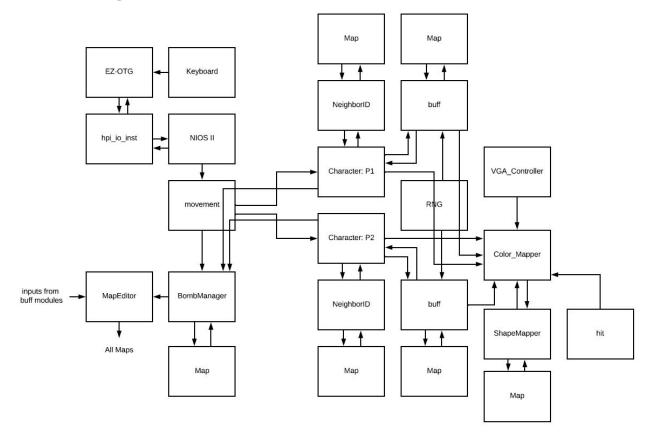

## **Description of Modules**

**Module:** VGA\_controller.sv **Inputs:** Clk, Reset, VGA\_CLK

Outputs: VGA HS, VGA VS, VGA BLANK N, VGA SYNC N, [9:0]DrawX, [9:0]DrawY

**Description:** This module outputs data to the VGA port. **Purpose:** Control the VGA port and anything connected to it.

Module: timer\_64Hz.sv Inputs: Clk, slow\_clk Outputs: [11:0]timer

**Description:** This module is a counter that increments on the rising edge of slow\_clk. **Purpose:** Other modules can use the output of this module to keep track of the time.

**Module:** ShapeMapper.sv

**Inputs:** [ADDR\_WIDTH-1:0]raddr, clk **Outputs:** [DATA WIDTH - 1:0] q

**Parameters:** ADDR WIDTH = 10, DATA WIDTH = 9

**Description:** This module maps each ID on the spritesheet to characters, bombs and all other

figures.

**Purpose:** Display correct shapes on the monitor.

Module: ScoreBoard.sv

**Inputs:** Clk, Reset, p1gain, p2gain **Outputs:** [7:0]p1score, [7:0]p2score

**Description:** This module calculates the score of each player (in decimal).

**Purpose:** Display correct scores on the monitor.

**Module:** RNG.sv

Inputs: Clk, Reset, [15:0]seed

**Outputs:** [3:0]randhex

**Description:** This module takes a 16-bit seed and generates an integer between 0 and 15 every

clock cycle. The algorithm used is linear feedback shift register.

**Purpose:** Generate a random 4-bit number for use.

**Module:** queue.sv

**Inputs:** [DATA\_WIDTH-1:0]in, we, Clk, Reset, next **Outputs:** [DATA\_WIDTH-1:0]out, empty, full

Parameters: ADDR WIDTH = 8, DATA WIDTH = 8

**Description:** This module generates a FIFO data structure with suitable data width.

**Purpose:** This module is used to store bomb information which is waiting to be processed.

**Module:** movement.sv

**Inputs:** [15:0]keyA, [15:0]keyB, [15:0]keyC

Outputs: [7:0]p1move, [7:0]p2move, p1bomb, p2bomb

**Description:** This module analyses the 6 input keycodes, and set the outputs based on the last

effective keys.

**Purpose:** Send keycode information to the correct modules.

**Module:** Map.sv

Inputs: [ADDR\_WIDTH-1:0]waddr, [ADDR\_WIDTH-1:0]raddr, [DATA\_WIDTH-1:0]wdata,

we, clk

Outputs: [DATA WIDTH - 1:0]q

**Parameters:** ADDR WIDTH = 8, DATA WIDTH = 8

**Description:** Simple duo-Port RAM with different read/write addresses and single read/write

clock and with a control for writing single bytes into the memory word.

**Purpose:** Initialize the map on the monitor.

Module: MapEditor

Inputs: WE0, WE1, WE2, WE3, WE4, WE5, Clk, Reset, ROM\_Clk,

[7:0] addr0, addr1, addr2, addr3, addr4, addr5, data0, data1, data2, data3, data4, data5,

Outputs: WE, [7:0] MapWriteAddr, [7:0] MapWriteData

**Description:** This module contains a state machine, a multi-input queue, and a ROM that stores

the initial map.

**Purpose:** This module is used to handle reset requests and all write-to-map requests.

Module: NeighborID

**Inputs:** [9:0]X Pos, [9:0]Y Pos, [9:0]Step, [7:0]waddr, [7:0]wdata, we, clk,

Outputs: up, down, left, right

**Description:** This module constantly read from the map to get the IDs of the items surrounding a

player.

**Purpose:** Determines whether the player is allowed to move further in a direction.

**Module:** hpi io intf.sv

Inputs: Clk, Reset, [1:0]from\_sw\_address, [15:0]from\_sw\_data\_out, from\_sw\_r, from\_sw\_w,

from sw cs, from sw reset

Outputs: [15:0]from sw data in, [1:0]OTG ADDR, OTG RD\_N, OTG\_WR\_N, OTG\_CS\_N,

OTG\_RST\_N

Inout: [15:0]OTG DATA

**Description:** Write data from EZ-OTG chip to NIOS II if writing is enabled. Otherwise, set high

Z.

**Purpose:** Interface between NIOS II and EZ-OTG chip.

Module: hit.sv

**Inputs:** Clk, Reset, p1gain, p2gain, [9:0]timer

Outputs: p1red, p2red

**Description:** p1red is set to high and kept for 0.5 second when p2gain is high. The same goes for

p2red and p1gain.

**Purpose:** Turn the character figure red when it gets hit.

**Module:** HexDriver.sv

**Inputs:** [3:0]In0 **Outputs:** [6:0]Out0

**Description:** This module transform a 4-bit number to a 7-bit number whose bits correspond to

the hexadecimal representation of the original number.

**Purpose:** Correctly displaying patterns corresponding to their values using the 7-segment

display blocks on board.

Module: explosion.sv

Inputs: clk, ready, player, [9:0]timer, [1:0]length\_in,[7:0]Data\_IN, [7:0]coordinate,

[3:0]randhex

Outputs: WE O, t,[7:0] Data O, [7:0] Address

**Description:** This is a state machine designed to edit the map as needed when a bomb is

supposed to explode.

**Purpose:** Create and clear the explosion effect, and place treasure chests based on the input

random number.

**Module:** ColorMapper.sv

Inputs: is Char1, is Char2, ROM Clk, dir1, dir2, p1red, p2red, [9:0]Char1 step,

[9:0]Char2 step, [1:0]bomb1 size, [1:0]bomb2 size, [9:0]delay1, [9:0]delay2, [9:0]cooldown1,

[9:0]cooldown2, [9:0]DrawX, [9:0]DrawY, [9:0]Char1 X Pos, [9:0]Char1 Y Pos,

[9:0]Char2 X Pos, [9:0]Char2 Y Pos, [7:0]p1score, [7:0]p2score, [23:0]defaultRGB

Outputs: [7:0]VGA R, [7:0]VGA G, [7:0]VGA B

**Description:** This module sets colors for all the items, characters, and maps.

**Purpose:** Display items, characters, and maps with the correct color on the monitor.

Module: Character.sv

Inputs: Clk, Reset, frame\_clk, [9:0]DrawX, [9:0]DrawY, [9:0]X\_Reset, [9:0]Y\_Reset,

[9:0]Step, [7:0] move, upID, downID, leftID, rightID

Outputs: is Char, [9:0]Char X Pos, [9:0]Char Y Pos, dir

**Description:** Updates character's position and movement every time the screen refreshes.

**Purpose:** Control character movement based on keypress ([7:0]move). Outputs is\_Char and dir are used to help Color mapper display the character correctly. Char\_X\_Pos and Char\_Y\_Pos are used in other modules.

Module: buff.sv

Inputs: Clk, Reset, player, [7:0]id, [3:0]randhex

Outputs: WE, [9:0]step, [1:0]size, [9:0]delay, [9:0]cooldown

**Description:** This module generates buffs or debuffs for both characters. **Purpose:** Add more elements to the game and make it more enjoyable.

Module: BombManager.sv

**Inputs:** Clk, Reset, p1bomb, p2bomb, [9:0]timer, [9:0]cooldown1, [9:0]cooldown2, [9:0]delay1, [9:0]delay2, [9:0]Char1\_X\_Pos, [9:0]Char1\_Y\_Pos, [9:0]Char2\_X\_Pos, [9:0]Char2\_Y\_Pos, [7:0]id1, [7:0]id2, [1:0]p1size, [1:0]p2size, [3:0]randhex,

**Outputs:** WE0, WE1, WE2, WE3, p1gain, p2gain, [7:0]addr0, [7:0]addr1, [7:0]addr2, [7:0]addr3, [7:0]data0, [7:0]data1, [7:0]data2, [7:0]data3

**Description:** This module is made of a state machine and other helper modules including queue and explosion. The state machine is used to handle all "placing bomb" requests, store bomb informations and provide necessary inputs for the explosion modules to function correctly.

**Purpose:** Handles all bomb-related tasks.

Module: BomberMan top.sv

Inputs: CLOCK 50, [3:0]KEY, [15:0]SW, OTG INT

Outputs: [6:0]HEX0, [6:0]HEX1, [6:0]HEX2, [6:0]HEX3, [6:0]HEX4, [6:0]HEX5, [6:0]HEX6, [6:0]HEX7, [7:0]VGA\_R, [7:0]VGA\_G, [7:0]VGA\_B, VGA\_CLK, VGA\_SYNC\_N, VGA\_BLANK\_N, VGA\_VS, VGA\_HS, [1:0]OTG\_ADDR, OTG\_CS\_N, OTG\_RD\_N, OTG\_WR\_N, OTG\_RST\_N, [12:0]DRAM\_ADDR, [31:0]DRAM\_DQ, [1:0]DRAM\_BA, [3:0]DRAM\_DQM, DRAM\_RAS\_N, DRAM\_CKE, DRAM\_WE\_N, DRAM\_CS\_N, DRAM\_CLK

**Inout:** [15:0]OTG\_DATA

**Description:** This is the top level of the whole project.

**Purpose:** Connect all modules together and make them work as expected.

# **Problems Encountered**

#### How to generate (pseudo) random numbers?

The first solution we thought of is to use the RNG functions in C. We would set up an Avalon MM slave, and modify our C code such that every time the software reads the key press, it also generates a random number and write it in the memory mapped register.

However, the C code is slow, so we do not want to give it too much work to do. Besides, we do not need a super good RNG since we are only using it for some add-ons in our game. Therefore we decided to write a hardware RNG. After doing some research on popular RNG algorithms, we chose to use linear feedback shift registers, which are easy to write and very widely used.

/testbench/Clk	1							
/testbench/Reset	0							
<u>→</u> /testbench/randhex	1110	1000	0101	(0000	1110	0100	(0110	)
<u>→</u> /testbench/zerocount	1240	1233	1234		1235		1236	5
+	1245	1236		1237				
+ /testbench/twocount	1267	1260				1261		)(
+ /testbench/threeco	1246	1242						
	0000000100100011	000000010	0100011					

Note: the four "counts" are used to keep track of the bit pattern of the last 2 bits fo output. It can be seen from the simulation that the four bit patterns (00, 01, 10, 11) appeared roughly the same times.

#### How to handle multiple "write to map" requests?

Our map (aka game board) is stored in on-chip memory, so it can only handle one write request per clock cycle. However, we have multiple elements that need to edit the map. A simple solution is to discard all other write requests except the one with highest priority. This approach would mostly work fine since humans are much slower than the system running at 50 MHz, so it is unlikely for multiple write requests to occur at the same clock cycle.

Rather than assuming the problem would never occur, we would like to actually solve the problem. Starting from a FIFO data structure, we implemented a multi-input queue. Every clock cycle, it puts all the inputs (at most 6) into a queue and pass them out one by one. We made the queue long enough so that it is unlikely to overflow.

### How do we know if a player scores and how to keep track of the scores?

It is stated in our rules that a player gets one point when the opponent is inside the affected area when a bomb explodes. Therefore we cannot simply check if a player is on a block with "explosion visual effect ID" and edit scores every clock cycle, as that may result in players getting multiple points from one explosion. What we ended up doing was to check players' positions when a bomb explodes and writes the visual effect to the map. Since this action only

happens once per explosion, we can be sure that players scores increment by at most one each time.

#### How and when do we add power-ups to the map?

Simple answer: add them randomly. But the hard problem is what the trigger for a "random test" should be. We came up with several possible solutions:

- (1) Every clock cycle or frame\_clock cycle, check the RNG to see if an item should be generated. If so, use another RNG to determine the location of the generated item. The problem of this approach is that both clocks are too fast, so that we need a very low success rate when running the first "random trial" to avoid flooding the screen with items. Such a low success rate is only possible with a RNG that has long output width. Besides, the algorithm we used to generate random numbers may not be stable enough to handle such a heavy task perfectly.
- (2) Everytime a breakable wall is destroyed, generate a random item on that location. This feature is not very hard to implement, but the total number of items would be limited, and the game would not be so fun once all the items are used up. Therefore we were not quite satisfied with this solution either.
- (3) Items would randomly come out from bombs.

  This solution may not make much sense at first sight, but actually solves both problems that idea(1) and (2) have. We finally decided to use this approach. Furthermore, to increase playability, we added the rule that the items from one player's bomb can only be used by the other player.

### How do we design the scale of every grid?

Considering the fact that we have a 640\*480 screen to display our work, we need to divide the space properly to satisfy the following two requirements: every element in a grid should be clear enough for people to tell what they are; every character should have enough space to move around. Ideally, the dimensions should be equal to or slightly less that some integer power of 2 to make writing and reading easier. After consideration, we decide to make each grid 32\*32, which makes the whole screen 20\*15 grids. The left 15\*15 is for the game map while the rest 5\*15 is used to display useful information for players.

## **Design Resources**

LUT	6,857
DSP	0

BRAM	2,322,432 bits			
Register	3,516			
Frequency	57.01 MHz			
Static Power	105.90 mW			
Dynamic Power	67.37 mW			
Total Power	262.11 mW			

# **Conclusion**

Final project is more helpful than any of our previous labs. We actually learn a lot and combine our knowledge to create such a work that we are proud with. It's like none of the previous labs where we just follow the procedure and things will be done correctly. This project has more design components than adding together all those included in labs. Every graph, every number, every move requires consideration. The question is not about how to make it functional but how to make it at least playable. Due to the time constraint and pressure from other courses, we were not able to finish all we think of. But after all, this is an unprecedented practice for us and the result is good enough. We know the experience of this project will help us a lot in the future.